The Tribune Radio—Comment and Advice—By Jack Binns

Receiver for Radio Known

This Is Title Bestowed on Super-Heterodyne System, One of E. H. Armstrong's **Epoch-Making Inventions**

Valuable on Short Waves

Reproduces Radio Telephone Speech Clearly Without Distortion or Howling

When E. H. Armstrong demonstrated his new super-regenerative system before the Radio Club of America, he made a comparative reference to the ber of inquirles regarding this system that I am going to give a brief out-


The super-regenerative is one of the och-making inventions of radio, and

Important on Short Waves Perhaps no better way of expressing this can be given than in the words used in the letters patent granted to Armstrong on June 8, 1920, which are

as 200 meters, but with only fair

How System Operates

Most Sensitive | Monarch of Radio Receivers-Armstrong's Super-Heterodyne | High Frequency | Radio To Be Used as Aid | Big Power Tube

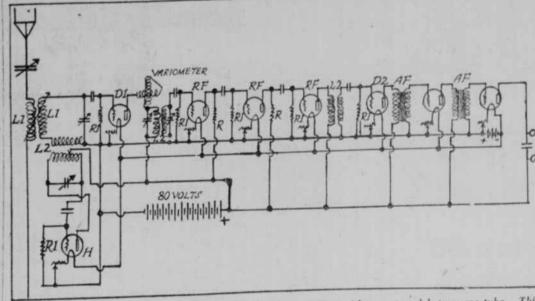


The diagram above shows a seven tube super-heterodyna receiver with an external heterouyne tube. This is the most sensitive and most selective receiver known at the present time. The coils LI are the primary and secondary tuned to short wave lengths. The coils L2 can be any form of oscillation transformer tuned to frequencies of 100,000 cycles per second, or in other words with a wave length range of 3,000 meters. The plate variometer is of the regulation short wave standard type and tunes the first detector for regeneration. The tube marked H is the heterodyne and the circuit about it is arranged to produce frequencies of 100,000 cycles. The combined frequencies of the incoming wave and the heterodyne tube ere converted to a lower frequency and amplified by the tubes marked RF. These tubes are shown in the diagram as resistance coupled, the resistances marked R having a value of 100,000 ohms. The resistances shown as RI are grid leaks and have a resistance of 5 megohms. The diagram shows two stages of audio frequency amplification after the second detector tube which is marked D2.

from seven to nine vacuum although there is no theoretical to the number that can be used to sthe number that enabled Paul to successfully receive no less to successfully receive no less

Super-regenerative Troubte

The control principle of the same in determinate by the control principle of the same in determinate by the control principle of the same in determinate by the control principle of the same in determinate by the control principle of the same in determinate by the control principle of the same in determinate by the control principle of the same in determinate by the control principle of the same in determinate by the control principle of the same in determinate by the control principle of the same in the grade of the

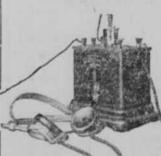

Hints for Those Wishing to System Radio Frequency | Amplification of Signals

System Not Perfect Yet

But Offers Scope for Those With Time and Means to Carry Out Experiments ter

Amplification Bureau of Mines to Work on Problem of Apparatus

Electric Light Plug Aerials Should Be Chosen With Care

Construction of Condenser Inside .Plug Important: for Safety They Should Withstand Line Voltage

In Mine Rescue Work Being Constructed, Marconi Declares

Working Tips

for This Purpose
The Bureau of Mines of the Department of the Interior is engaged in studying the problem of applying and apparatus in conjunction with Experiment With Cascade in cases of emergency. One of the

Improving Faulty Crystal



AntennaWire

MagnetWire



amplification in short waves is for the experimenter who has time and means to work with it. Only hard tubes can be used in connection with it. These tubes, of course, are not critical as to plate voltage, and at least 45 volts should be used in the plate circuits.

The potentiometer should be varied very carefully until the best signal results are obtained. The more the potentiometer is varied toward the positive side the more stable the set will operate, but the signals will be weaker. The more negative bias put on the grids by the potentiometer the stronger the signals will be until the oscillating point is reached. The set should be kept below this point.

In the Making the Most of Radio

UBILIER radio products have been accepted as the standard equipment by the principal radio companies and governments of the world. All of them help you to make the most of radio. They are scientifically designed and carefully manufactured, so that, for their particular purpose, they have an unrivalled their particular purpose, they have an unrivalled

Music From Any Lamp Socket The Dubilier Ducon does away



with the outside antenna and indoor loop. Simply screw it into any electric-light socket, connect it with any standard receiving set, and you hear broadcasted concerts perfectly.

The Dubilier Ducon is tested to withstand a breakdown voltage of 2500. It is the only absolutely safe device of its kind.

Dubilier Micadons Reduce Tube Whistling Dubilier Micadons are little mica

Licensees for Canada: Canadian General Electric Company, Toronto



condensers which improve reception because they are permanent in capacity. If your set is not equipped with Micadons you are not hearing the broadcasting station at its best. They are supplied with and without grid-leak mounting. They do away with much

Price 35 cents of the tube howling and whistling that Dubilier Micadons vary in

price from 35 cents each to one dollar each, according to capacity. Ask your dealer



Dubilier Condenser & Radio Corp. 48-50 West Fourth Street, New York

Daily Radio Program

Sunday, July 23

Beware of Imitation!

"ALL WAVE" Coupler

Eliminates the use of Vari Loading Coils.

Guaranteed Wave Length 150 to 3000 Meters

List \$9.00

Capitol Phonolier Corp. 56 Lafayette St. New York,



SAME quality as sold every-where at \$12 to \$15. Our own regular price is \$9. But we are making a special in-troductory price of \$6.50 for a limited period.

High grade rubber composition cap-aluminum backs, black waves band covering, navy standard adjustment Remissance 2200 ohrus. Single phone \$3.75. Insist on TENTOR at your dealer's or order direct from us. Pay post-man \$6.30 on delivers.

TEKTOR CORPORATION 250 W. 57th St., New York

Radio Books ALL UP TO DATE

We publish a full line of Radio and Automobile Books as well as Books on more than fifty dif-ferent subjects. FREE Send for special circular at our stadio Books and for rathfogue of all our practical publics.

Norman W. Henley Pub. Co. 2 West 45th St., New York

12000 OHM RESISTANCE UNITS ARMSTRONG SUPER REGENERATIVE

CIRCUIT The Prometheus Electric Co Rocky Mountain Crystak

Mounted ISc Unmounted 10c Postpaid Rocky Mountain Radio Products, Inc. 9 Church St., New York N. Y. This offer expires July 51, 1931.

gnal Corps U. S. Army Vacuus (Western Electric) Types VI as he last word in efficient Receiving Hilling and Amplifying Tubes. Gus Prices Reduced. All sets and supplies reduced in AMALGAMATED RADIO SUPPLY William St. Phone 5225 B